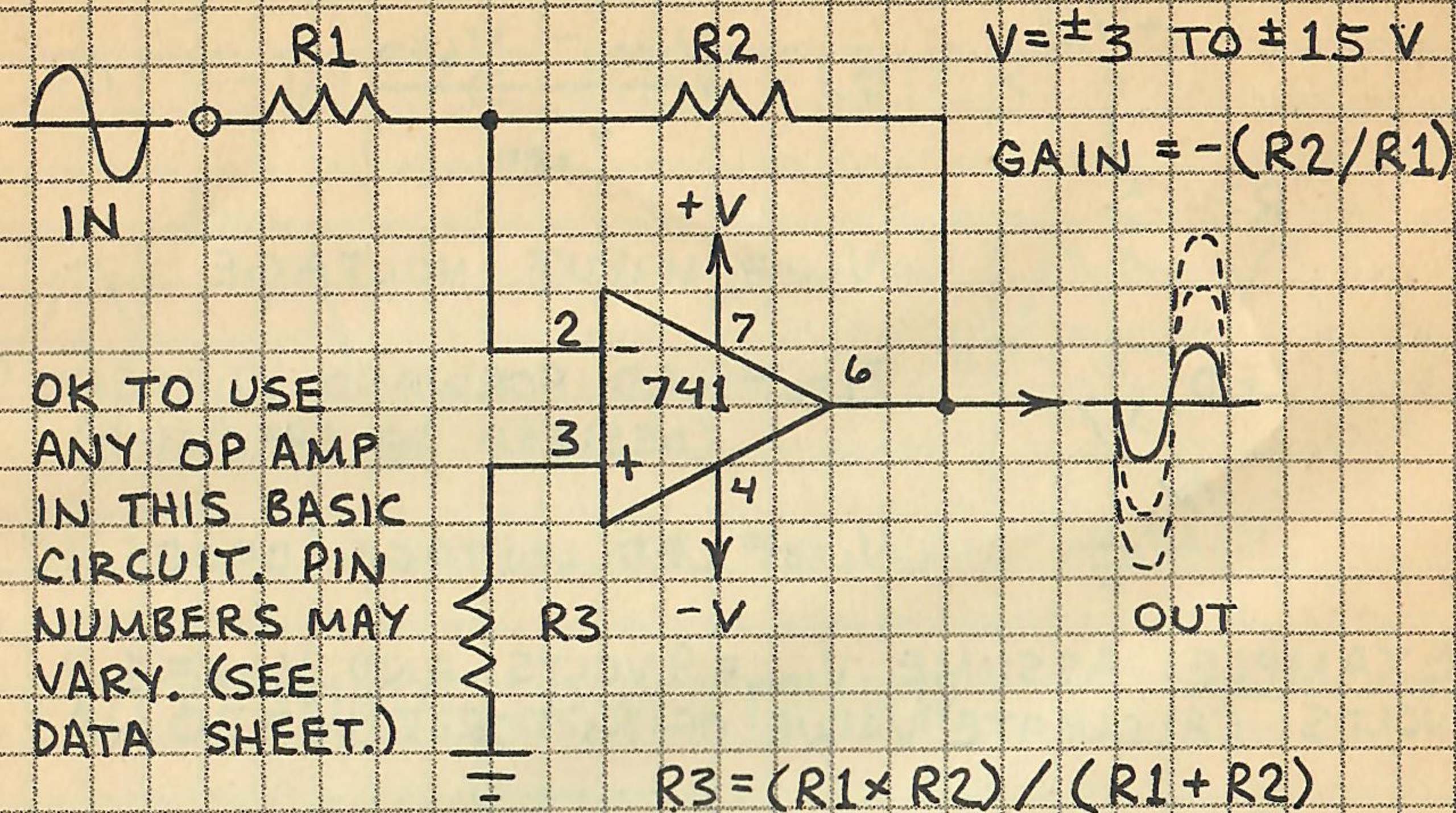



INVERTING AMPLIFIER



OK TO USE ANY OP AMP IN THIS BASIC CIRCUIT. PIN NUMBERS MAY VARY. (SEE DATA SHEET.)

EXAMPLE: IF $R1 = 4,700 \text{ OHMS}$ AND $R2 = 47,000 \text{ OHMS}$, THEN GAIN IS $-(47,000/4,700)$ OR -10 . $R3 = 4,273 \text{ OHMS}$ (USE CLOSEST STANDARD VALUE).

NON-INVERTING AMPLIFIER

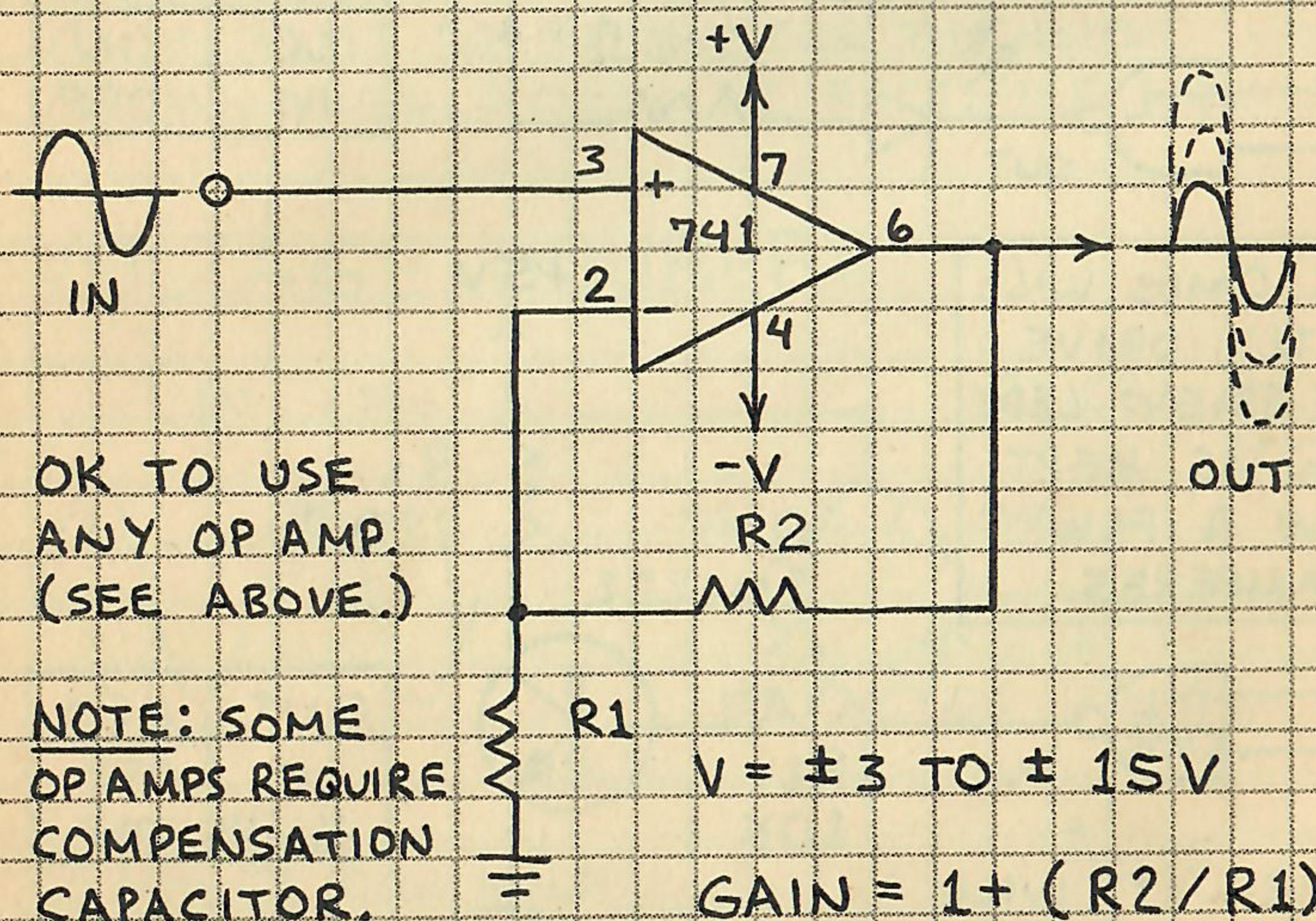


OK TO USE ANY OP AMP. (SEE ABOVE.)

NOTE: SOME OP AMPS REQUIRE COMPENSATION CAPACITOR.

EXAMPLE: IF $R1 = 4,700 \text{ OHMS}$ AND $R2 = 47,000 \text{ OHMS}$, THEN GAIN IS $1 + (47,000/4,700)$ OR 11 .

VOLTAGE-TO-CURRENT CONVERTER

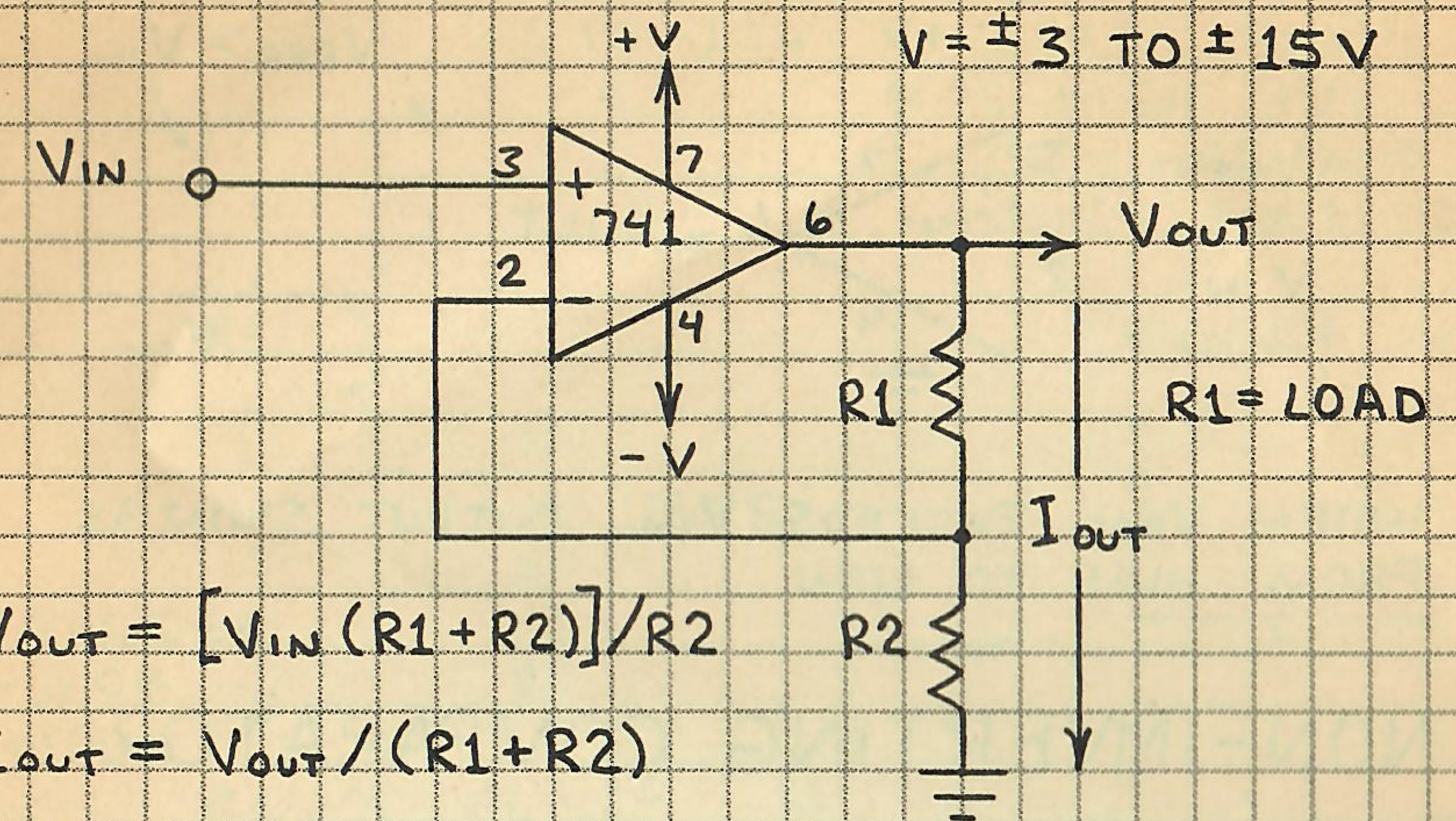


$$V_{out} = [V_{in} (R1 + R2)] / R2$$

$$I_{out} = V_{out} / (R1 + R2)$$

$$I_{out} = V_{in} / R2$$

EXAMPLE: ASSUME $R1$ IS A RESISTOR AND LED WITH COMBINED RESISTANCE OF $1,000 \text{ OHMS}$ AND $R2$ IS 470 OHMS . WHEN $V_{in} = 5 \text{ VOLTS}$, CURRENT (I_{out}) THROUGH LED IS 10.6 MA .

CURRENT-TO-VOLTAGE CONVERTER

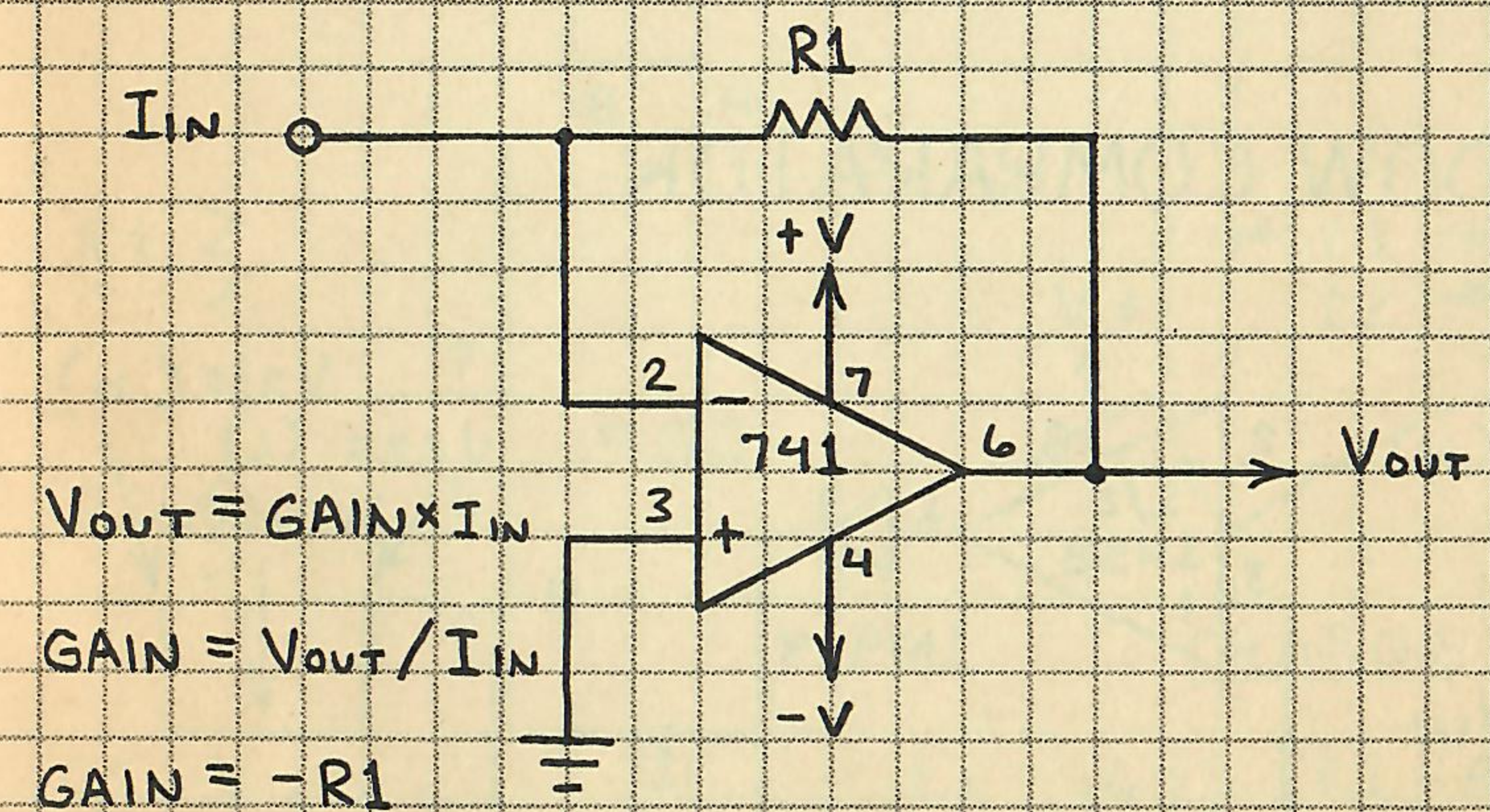

EXAMPLE: ASSUME A SOLAR CELL CONNECTED TO I_{in} DELIVERS A CURRENT OF 1 MA . IF $R1$ IS $1,000 \text{ OHMS}$, THEN $V_{out} = -(1,000 \times 0.001) = -1 \text{ VOLT}$.